



The Shirpur Education Society's
R. C. Patel College of Engineering and Polytechnic, Shirpur
Department of Electrical Engineering

NOTES

Programme Code: Electrical Engineering

Year/Scheme: EE3K

Semester: 3rd

Course Title: Fundamentals of Power
Electronics

Course Abbr.: FPE

Course Code: 313335

Subject Teacher :- Ms. H.A.Badgujar

UNIT-04 – (10 MARKS)

DC-DC Converters

CO Coverage: - Test the performance of given chopper.

Unit -04 Content (Syllabus)

- 4.1 Basic terminologies: duty ratio, turn on period, turn off period, chopping period.
- 4.2 Control strategies of chopper: Constant frequency system, variable frequency system.
- 4.3 Step up chopper: circuit diagram, working, waveforms and output voltage equation.
- 4.4 Step down chopper: circuit diagram, working, waveforms and output voltage equation.
- 4.5 Buck-Boost chopper: circuit diagram, working, Waveforms and output voltage equation.

4.1 - Basic Terminologies :-

1) Chopper :- The chopper circuit is power electronic circuit that converts fixed DC voltage at its input into a variable DC output voltage. Hence a chopper is known as DC to DC converter.

1) Duty ratio \Rightarrow (Duty Cycle) :-

Duty ratio of a chopper is defined as the ratio of turn on period (T_{on}) and the total time (T)

$$\text{i.e. Duty cycle} = \frac{T_{on}}{T}$$

where, $T = T_{on} + T_{off}$.

2) Turn ON period :- (T_{on})

Turn on time of chopper is defined as the time for which output voltage remains low. It is denoted by T_{off} .

3) Turn off period \rightarrow (T_{off}) The turn off time of chopper is defined as the time of which output voltage remains low. It is denoted by T_{off} .

4) Chopping Period :- It is defined as reciprocal of chopping frequency that means the frequency at which chopper is turn on and off.

* 4.2 Control strategies of chopper \rightarrow

The average output voltage can be controlled by following methods :-

- 1) Pulse width modulation (PWM) / Constant frequency.
- 2) Frequency modulation or variable frequency system.

* Pulse width modulation technique :-

\rightarrow In this controlled technique of chopper the total time period or frequency is constant. And we can vary the ON time of chopper to get a variable output voltage.

\rightarrow The average output voltage is directly proportional to the ON time of the chopper.

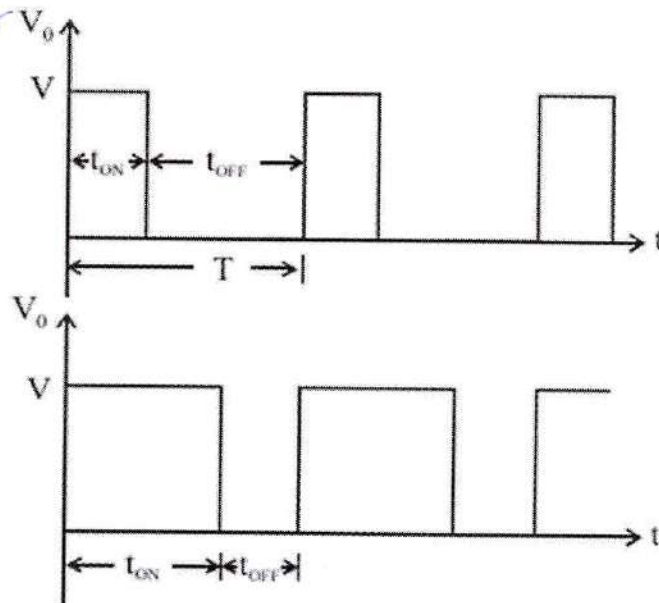


Fig. Pulse Width Modulation Control


\rightarrow In this technique we change the ratio of on time of the chopper to the total time. Hence it is also called as time ratio controlled (TRC) technique.

\rightarrow Fig. shows the output voltage waveforms for different ON times.

→ In PWM the pulse width (t_{ON}) of the output waveform is varied keeping chopping frequency ' f ' and hence chopping period ' T ' constant. Therefore output voltage is varied by varying the ON time, t_{ON} .

* Variable Frequency system or Frequency Modulation ⇒

- In this method, the ON time of chopper kept constant and variation in the average output voltage is obtained by varying the total time or chopping frequency.
- In this technique the ratio of T_{ON} divided by T , or Duty cycle is change by changing the T_{OFF} time of the choppers.
- This technique is called as frequency modulation technique.
- This type of control generated harmonics at unpredictable frequencies and the filter design would be difficult.

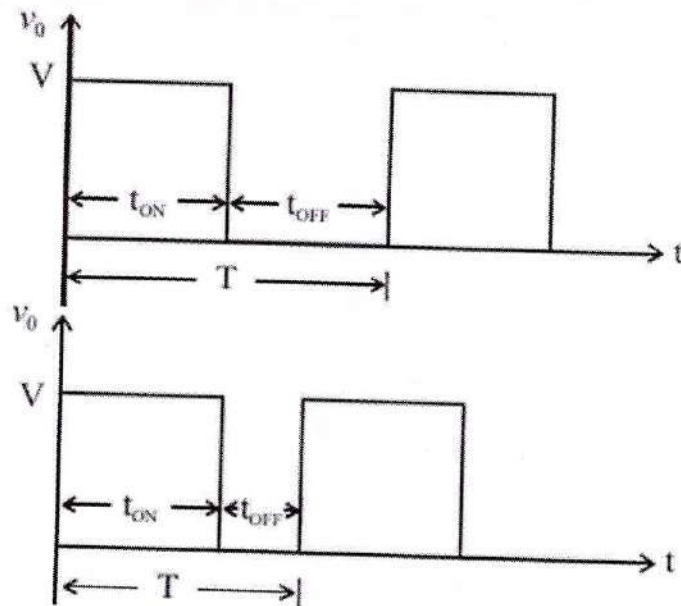

→ Fig. shows the output voltage waveforms for a constant t_{ON} and variable chopping period (T).
Fig. o/p voltage waveform

* 4.3 - step up chopper ⇒

Step up chopper is a type of chopper where output DC voltage is higher than i/p DC voltage. Step-up-chopper is also called as Boost chopper and it is classified as class B choppers.

* Operation ⇒ When the average output voltage is greater than the ~~chopper~~ input voltage is called as step up chopper.

→ Fig ① shows step ~~down~~ chopper and fig ② shows waveforms of step ~~down~~ chopper.

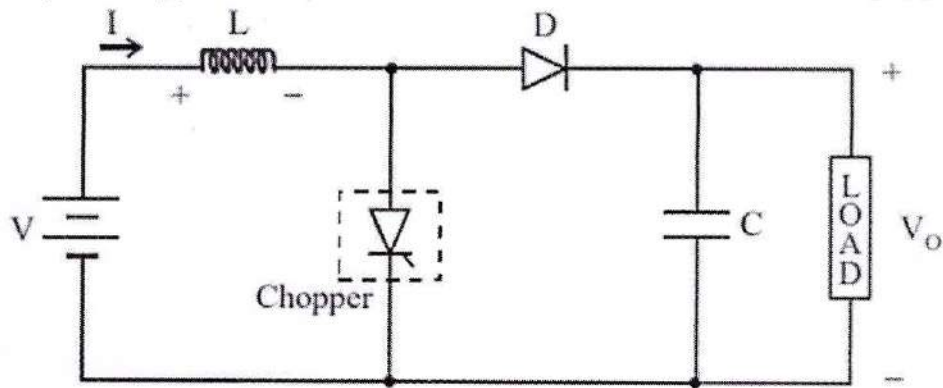


Fig. Step-up Chopper

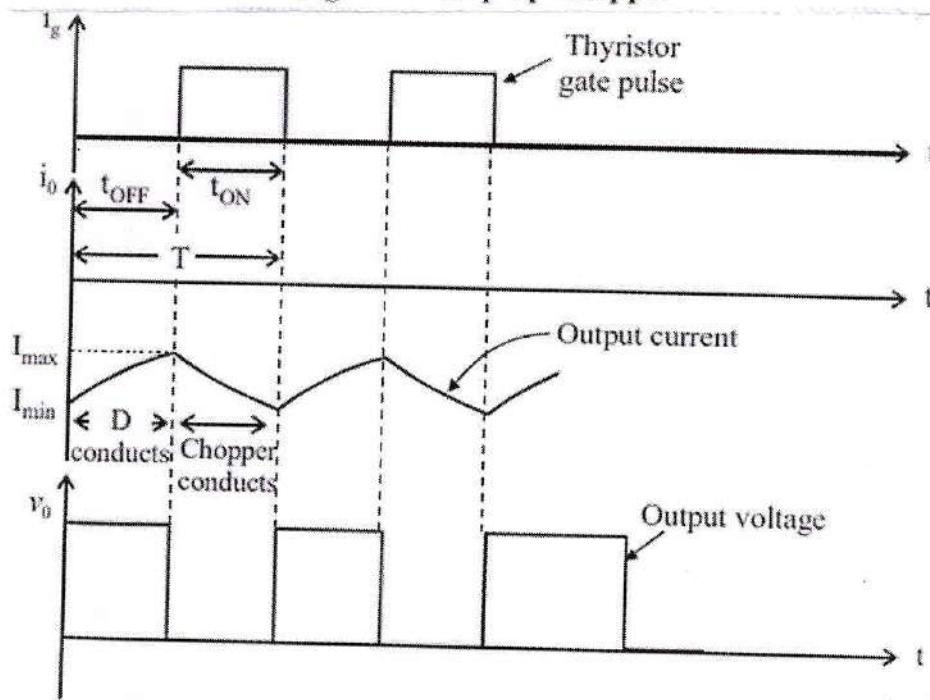


Fig. : Class B Chopper - Output Voltage and Current Waveforms

- In this chopper large inductor L in series with source voltage V_s essential as shown in fig.
- When the chopper CH is on the close path for current is input voltage source to the inductor to the chopper and back to the source.
- During this period the inductor stores large amount of energy for T_{ON} time.
- When chopper is off, diode D conducts, $V_o = V_s$ and a part of energy stored in inductor L is returned to the supply.
- As a result, the voltage across load is not only the source voltage V_s but also the inductor voltage $L \cdot \frac{di}{dt}$ (Discharging of inductor energy)

$$\text{i.e. } V_o = V_s + L \frac{di}{dt}$$

→ Hence, we can say, the output voltage is more than the input voltage V_s .

$$V_o = V_s + e_i \quad \dots \quad [e_i = \text{inductor stored energy}]$$

$$\text{i.e. } V_o = V_s + L \frac{di}{dt} \quad \therefore V_o > V_s$$

where $V_s =$ input voltage.

$V_o =$ output voltage.

$$V_o = \left[\frac{V}{1 - \frac{T_{on}}{T}} \right] = \frac{V}{[1 - D]}$$

* 4.4. Step down choppers :->

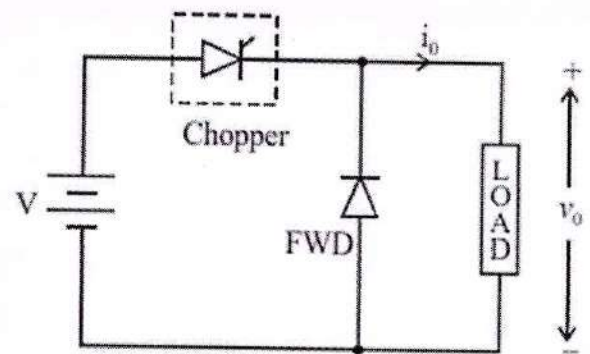


Fig. Class A Chopper

→ Above fig. shows the circuit diagram for step down choppers with R-load. This chopper circuit is also called as class A choppers.

→ This chopper works in first quadrant. i.e. The output voltage and output current is always positive.

* operation :-


→ At $t = t_0$, the chopper switch is closed. This connects the input dc voltage across the load resistance.

→ Switch S is remains closed for time T_{on} . The input voltage V_s appears across the load.

→ The load current $= \frac{V}{R}$ and has the same shape as that of load voltage.

- At $t = DT$, the chopper switch is turned off. This will disconnect the input DC source from the load, making reducing
- the load voltage and load current to the zero.
- If the switch remains off for the period of T_{off} time. No output voltage and current will be there at the load.
- The sum of T_{on} & T_{off} gives the total time of the chopper.
- At $t = T$, where, the switch is turned on again and the operation repeats itself.

Fig. Class A Chopper o/p waveform.

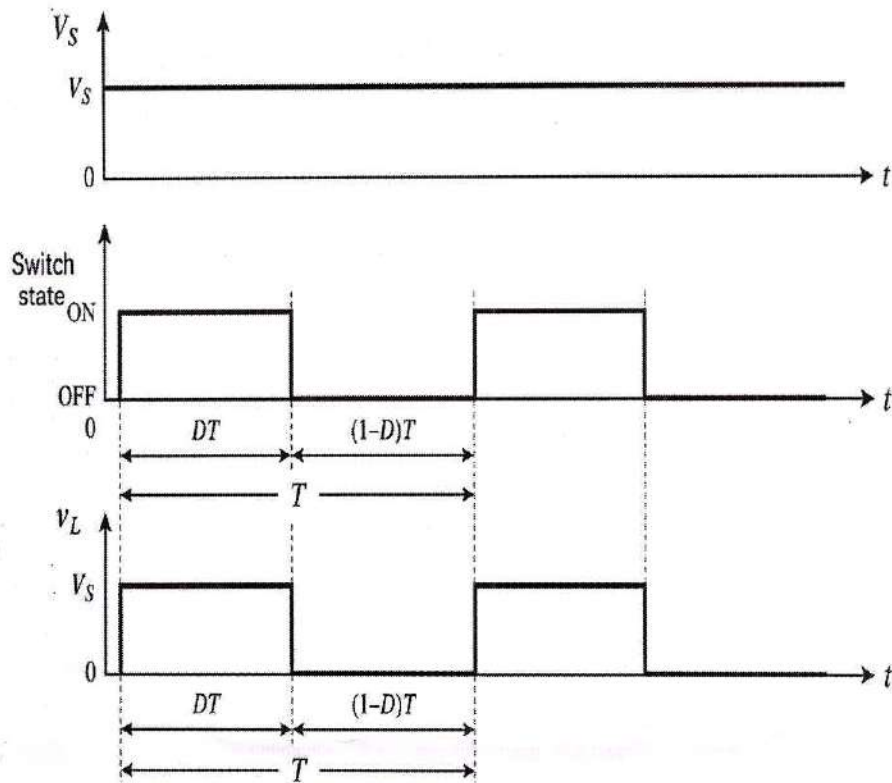

→ Average output voltage :-

$$V_{LDC} = \frac{1}{T} \int_0^{T_{on}} V_s \cdot dt$$

$$= \frac{V_s}{T} [t]_0^{T_{on}} = \frac{V_s}{T} [T_{on} - 0]$$

$$= \frac{V_s}{T} \cdot T_{on} = \frac{T_{on}}{T} \cdot V_s$$

$$\therefore V_{LDC} = D \cdot V_s$$

→ Average output current :-

$$I_L = I_o = \frac{V_{LDC}}{R} = I_o = \frac{D V_s}{R}$$

* 4.5 - Buck Boost Chopper :->


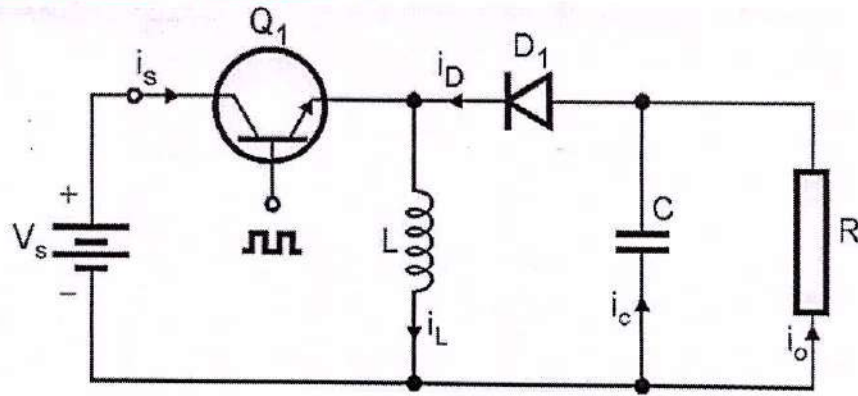


Figure 1: Circuit Diagram of Buck Boost Converter.

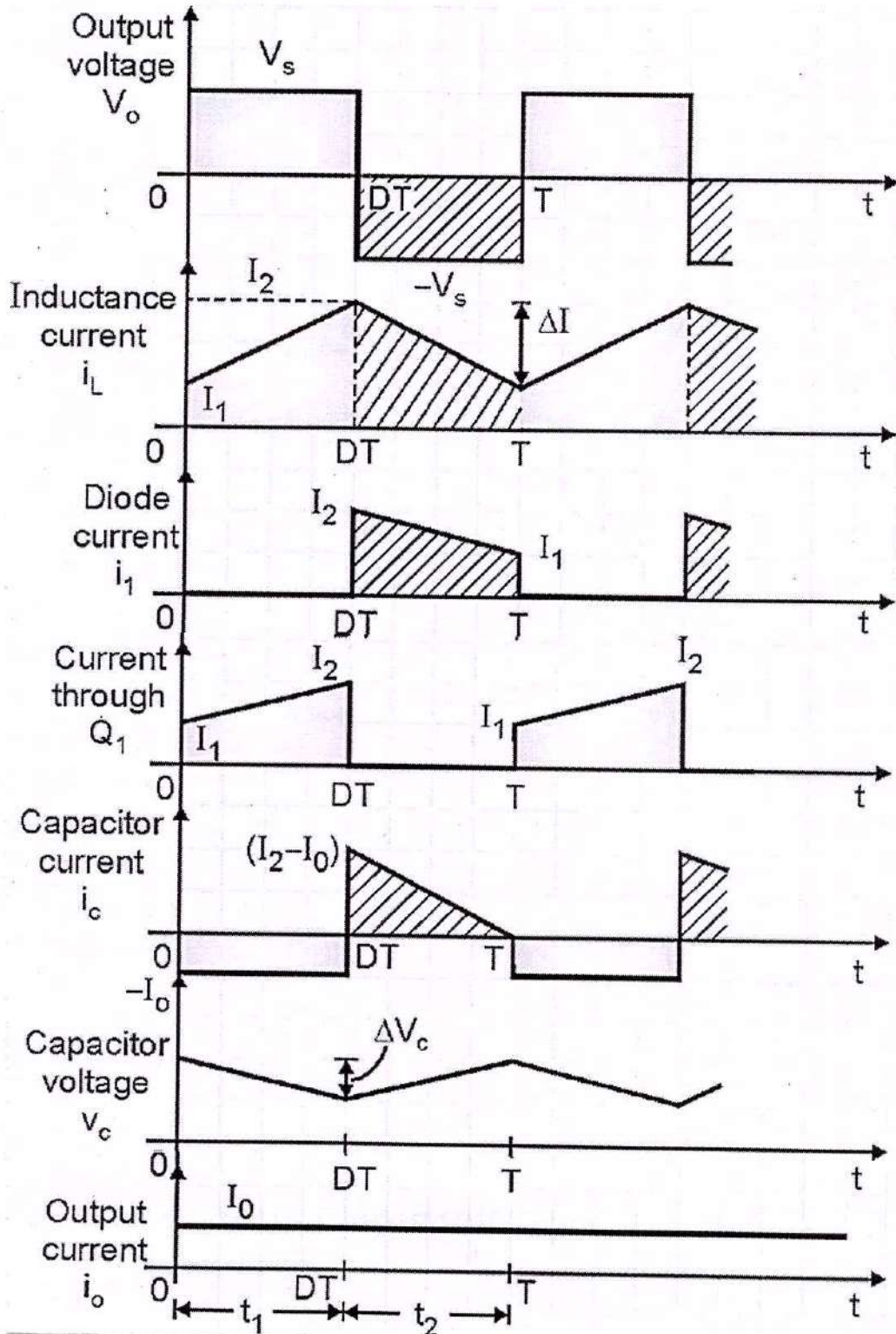

- The circuit diagram of buck-boost chopper is as shown in Fig. (1)
- The buck boost switching regulator is non isolator type converter & also known as inverting chopper.
- The buck-boost chopper is a type of flyback converter whose operation is very similar to boost regulator.
- A buck boost chopper provides an output voltage that can be either less than or greater than DC input voltage V_s .
- Hence the name given to it is buck boost. The O/P voltage polarities is opposite to that of I/P voltage. Therefore it is also known as inverting chopper.
- A power BJT is used as switching device, but it is possible to use either MOSFET or IGBT in the place of power BJT.

* Operation → mode-1 [Q_1 -ON, D_1 -OFF]

- At $T=0$, V_s gets connected across the inductance L and the diode D_1 is reverse biased.
- The inductor current starts increasing linearly from I_1 to I_2 .
- The energy get stored in the inductor during this mode of operation.

* mode-2 [Q_1 -OFF, D_1 -ON]

- Q_1 is turn off at $t = t_1$, the current through inductor L is interrupted abruptly.
- A negative voltage is induced into L which forward biased the diode D_1 .
- The load current starts flowing through D_1 , C & L . Note that this current is negative with respect to load.
- The capacitor charges with it's lower plate +ve w.r.t. upper plate.
- During this mode the energy stored in L is delivered to the load, and inductor current decreases from I_2 to I_1 linearly until transistor Q_1 is turned on again.
- This mode comes to an end when Q_1 is turned on again in the next cycle of operation.

* Comparison between Boost & Bulk Chopper.

Parameters	Boost	Bulk
1. Range of output voltage	V_s to above V_s	0 to V_s volts
2. Position of chopper switch	In parallel with Load	In series with Load
3. Expression for output voltage	$V_o = \frac{V_s}{(1-D)}$ volts	$V_o = V_s D$ volts
4. Quadrant of operation	2 nd quadrant	1 st quadrant
5. External inductance	Required for Boosting the output voltage	Not required
6. Application	Voltage Boosters	Motor speed control

* Features of Buck Boost Chopper :-

- 1) This circuit produces -ve output voltage.
- 2) It's efficiency is high.
- 3) Input current is discontinuous.
- 4) It's easy to implement short circuit protection.
- 5) High peak current flow through transistor.

* Applications of chopper :-

- 1) DC motor speed control
- 2) DC voltage boosting.
- 3) Battery operated in electric cars.
- 4) Battery chargers.
- 5) Battery operated appliances.

QUESTION BANK/ASSIGNMENT -04

Course & Code: EE-3K

Semester: Third

Name of Subject: Fundamentals of Power Electronics

Subject Code: 313325

Que. No.	Unit 4 DC-DC Converters (10 Marks)	Exam	Marks
1	Define: (i) Duty cycle (ii) Chopping period w.r.t. chopper	W-24	2
2	List any two applications of chopper.	W-24 W-25	2
3	Explain operation of step-up chopper with neat circuit diagram.	W-24	4
4	Describe working of step-down chopper with neat circuit diagram and waveforms. Also write formula for O/P voltage.	W-24 W-25	6
5	State the need for pulse width modulation used in inverter and list its types.	W-25	4
6	Draw and explain the operation for step down chopper.	W-25	4
7	Explain the terms related to Chopper : (i) Turn on period (TON) (ii) Turn off period (TOFF)	S-25	2
8	Define a photovoltaic (PV) cell.	S-25	2
9	Compare Step up and Step down chopper	S-25	2
10	Explain variable frequency control strategy of a chopper along with output waveform	S-25	4
11	Draw the block diagram and explain the operation of a wind power generation system	S-25	4
12	Describe working of step down chopper with neat circuit diagram and waveforms. Also write equation for output voltage.	S-25	4
